

- Please fill out below (pre) survey for the class
 - <https://forms.gle/PaF862gYxhfhfTVw7>
- Please register to AMD
 - <https://www.amd.com/en/registration/create-account.html>
 - Could need to download free license
- Please take workshop photos and share here
 - <https://photos.app.goo.gl/PwyXYC5XvxowUsU6A>
 - If you want a photo deleted, let me know.
 - Album will be destroyed at Sep. 30, 2025

Groups

Please let me know if you want to change your group

Some Experience
오준원
홍지은
어윤
허우현
김연주

Screen

HLS /Windows
채지완
태봉호
허지원
김우종
정진룡

Linux /Macbook
안치환
오민석
김총
안근필
최성준

Macbook
김영완
장하은
김지연
전우철
권도훈

Group Icebreaking (15 min, 2 min per person)

- Please gather by groups
- Please introduce yourself
 - Name, University, Career stage: Student/Ph.D/Scientist/Faculty
 - What research do you do?
 - What experience you have had with FPGAs?
 - Why did you come to the workshop?
 - What do you like to do (Hobby)? What did you do during summer? Anything fun/special?

Introduction to FPGA

Outline



- What is a FPGA?
- What is firmware?
- Workflow of creating firmware

What is a Field Programmable Gate Array (FPGA)?


- Can be used in many fields: HEP, Communication, Aerospace, ...
- Can be reprogrammed to change to meet specific needs.
- Has array of components, where connections can be modified.

Global FPGA Market

Share, By End-Use, 2023 (%)

 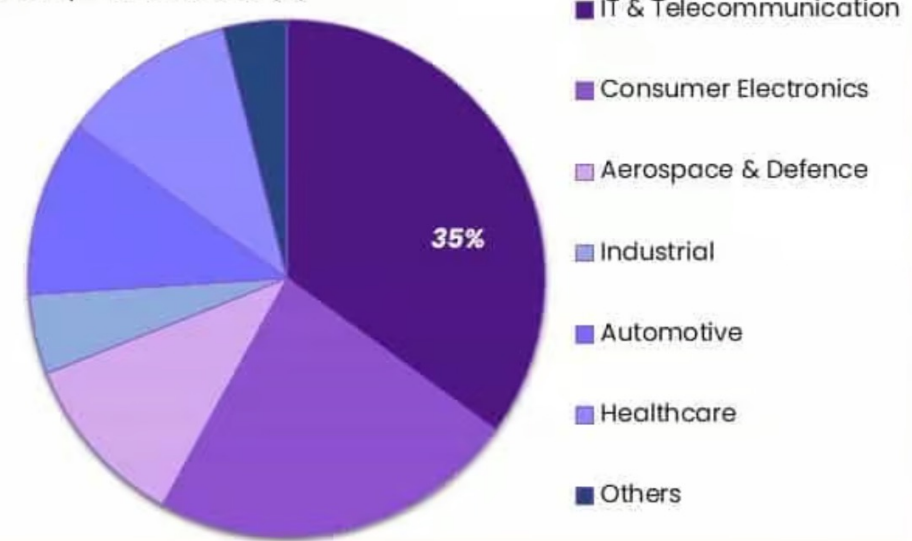



(a) Before making connections

 

 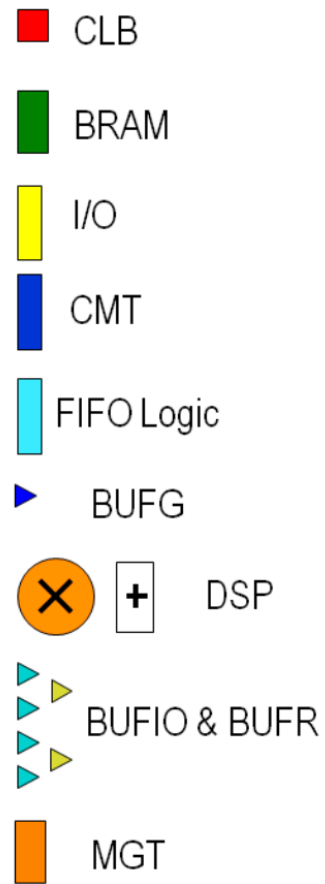(b) After connections made

What is inside a FPGA?


- CLB: Configurable logic block
- BRAM: Block RAM
- CMT: Clock management tile
- DSP: Digital Signal Processor



Components/Resources of FPGA

What is a configurable logic block (CLB)?

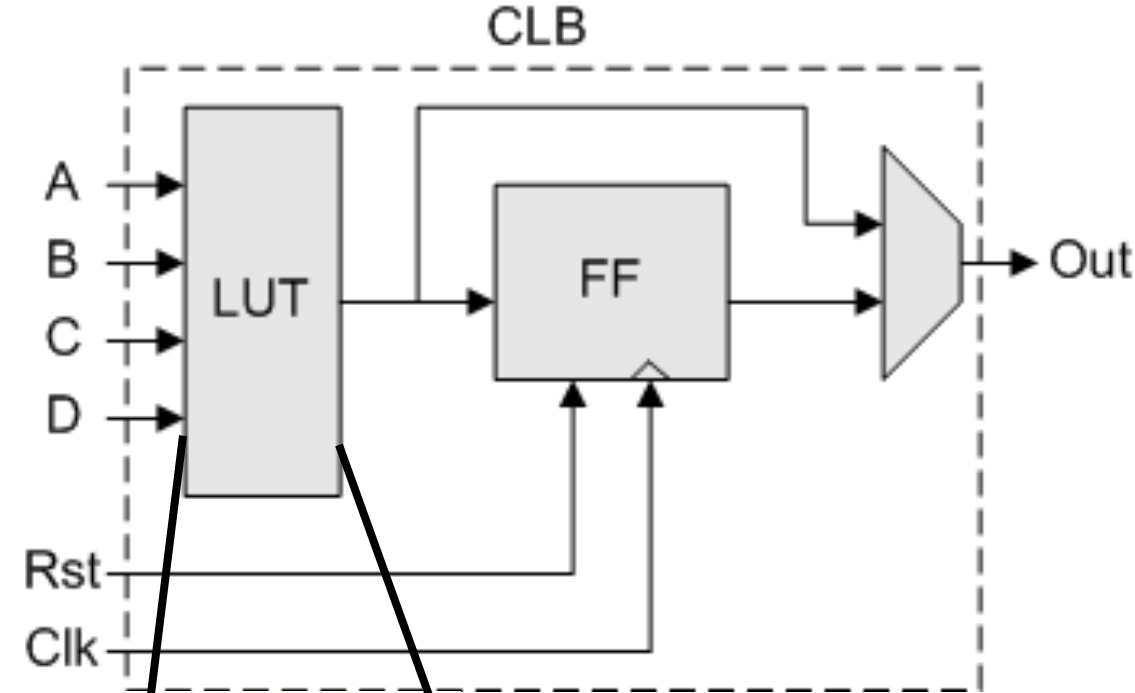
- Contains configurable Look-Up-Table (LUT)
- Flip-Flop (FF): Can store data ("0", "1") for a period of time



Truth Table

Inputs				Output
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0


How can configurable LUT be used?

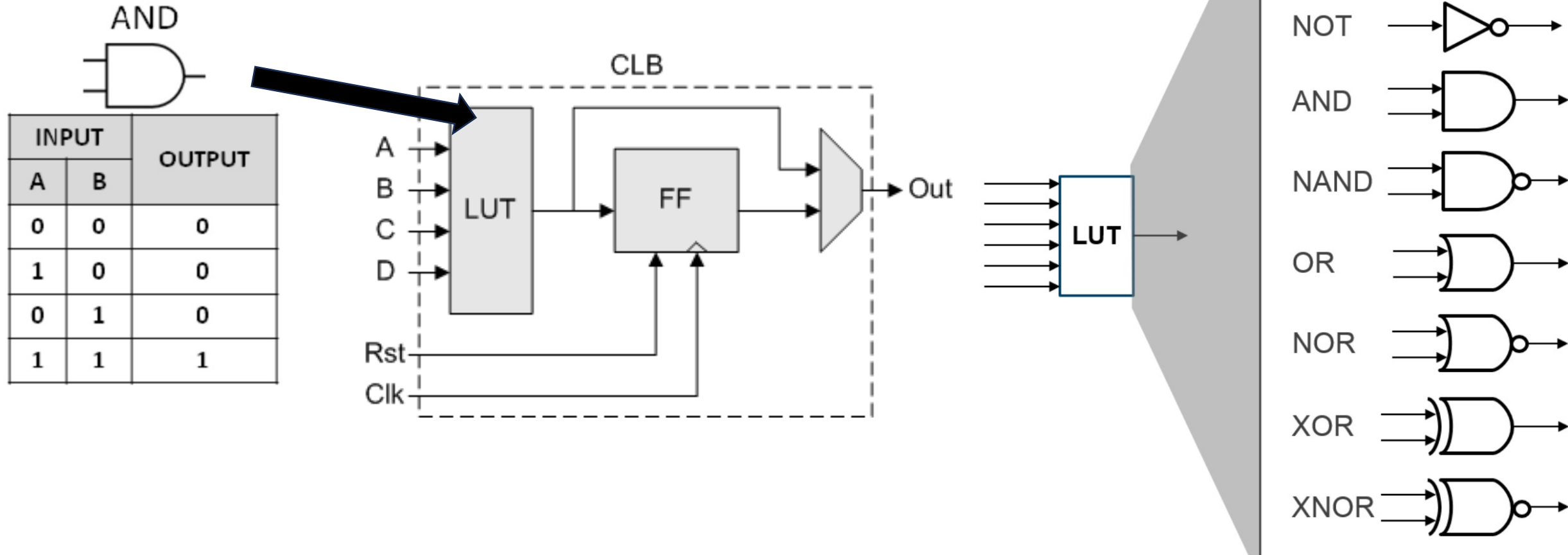

- Configurable LUT can be used as digital logic gates.


How are resources connected?

 - Interconnect wires resources together.
- Reprogrammable switch used to change FPGA functionality.



Implementing digital logic

 - There is a digital circuit called “Half adder”



XOR table

A	B	Out
0	0	0
1	0	1
0	1	1
1	1	0


Half adder table

A	B	S	C
0	0	0	0
0	1	1	0
0	1	1	0
1	1	0	1

- Half adder adds up one bit inputs.



Half adder with transistors and resistors

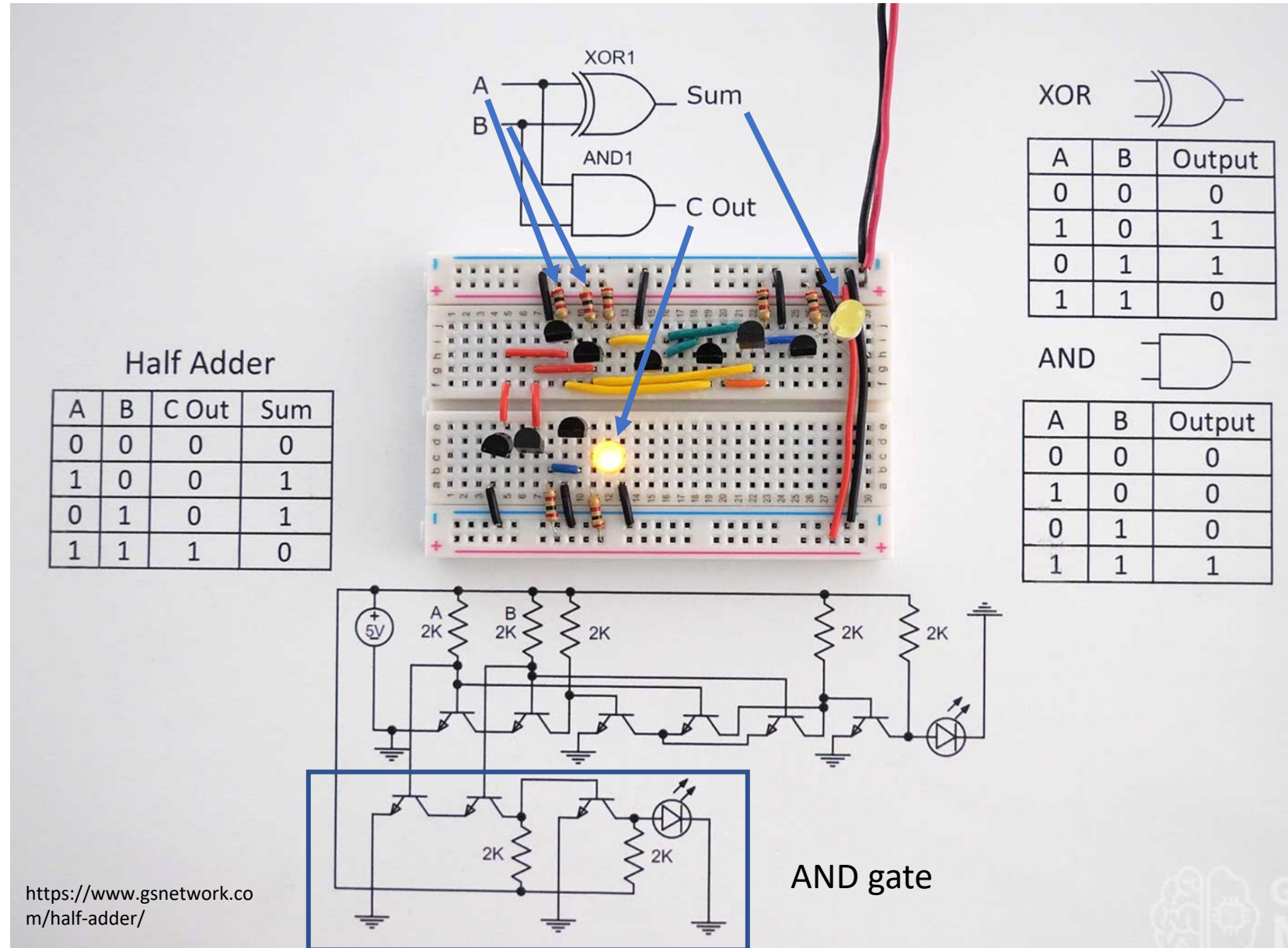- Can make with transistors and resistors.
- When resistors are connected "1".
- LED shows the output. On is 1.



Half adder with transistors and resistors

  - Input A and B can be set by connecting resistors to 5V.
- But it takes time for the signal to pass through the transistors.





Differences with C++

C++ code



```
Sum = !A != !B;  
Carry = A & B;
```

  - C++ runs in a sequence
 - Gates run in parallel for circuits/FPGA
- C++ doesn't need to consider timing
 - Need to consider timing for circuits/FPGA.




Half adder with transistors and resistors

  - Input A and B can be set by connecting resistors to 5V.
- But it takes time for the signal to pass through the transistors.
- **This can be a problem.**



Issue of different timing

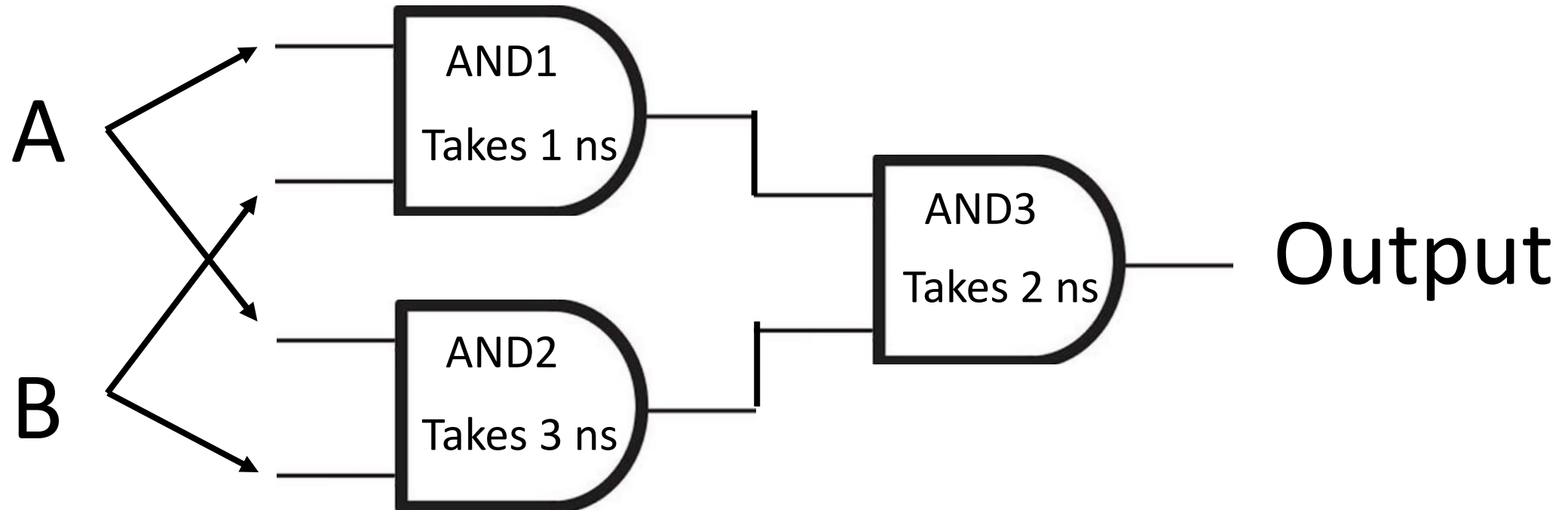
- What if we have circuits with different timing.



- When and how will output change?

Issue of different timing


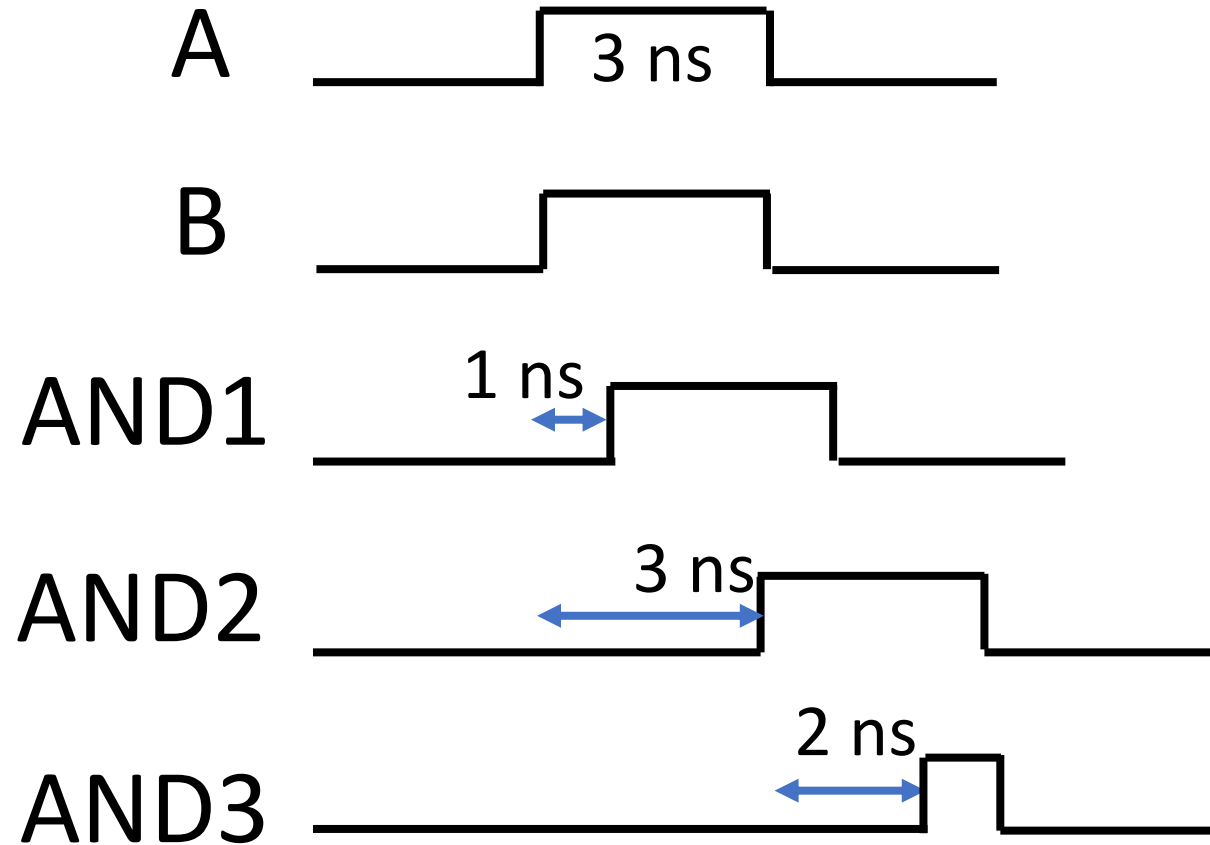
- What if we have circuits with different timing.




- AND3 width is only 1 ns. Can be issue when more logic.

How can this timing issue be resolved?

  - Output of circuits can be saved using flip-flops (FF).
- Input data is only saved at rising clock edge.




Circuit with flipflop (FF)

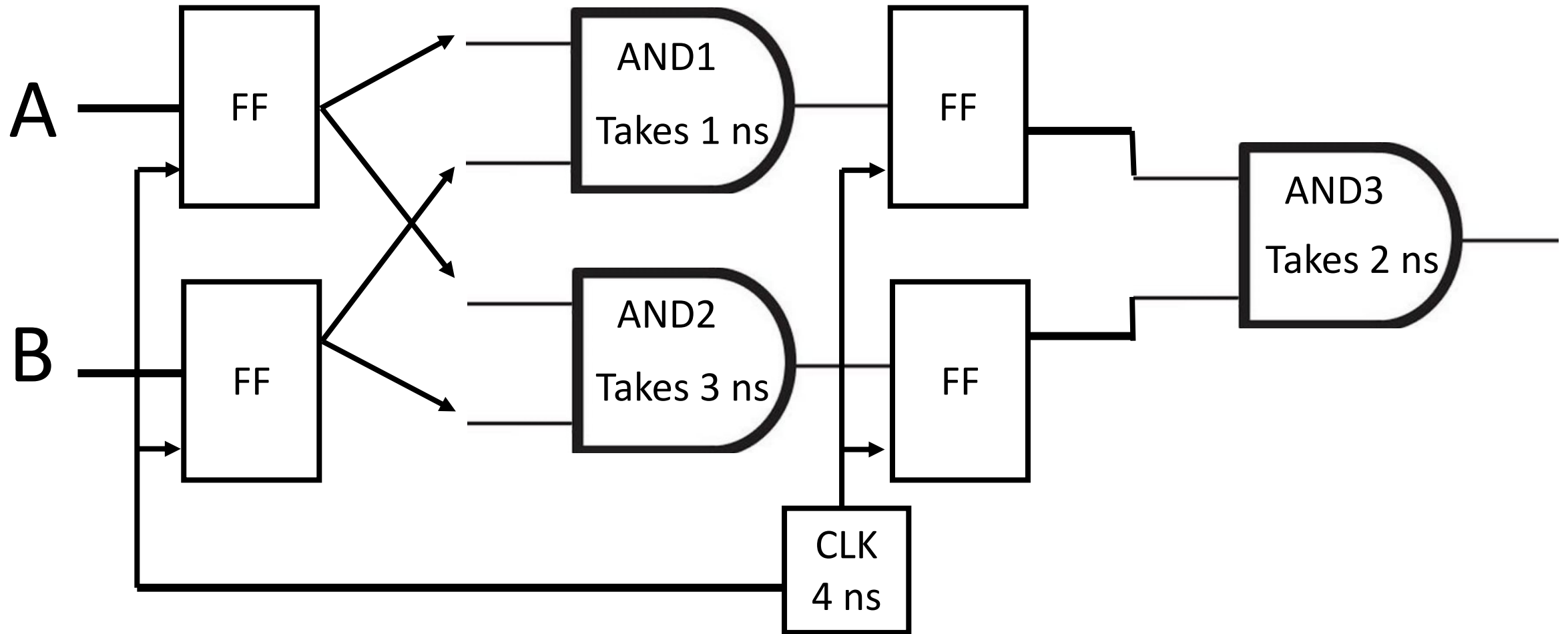



- Flip flops can be added between circuits.
- FF changes only at 4 ns at clock.

Timing of logic with flipflops

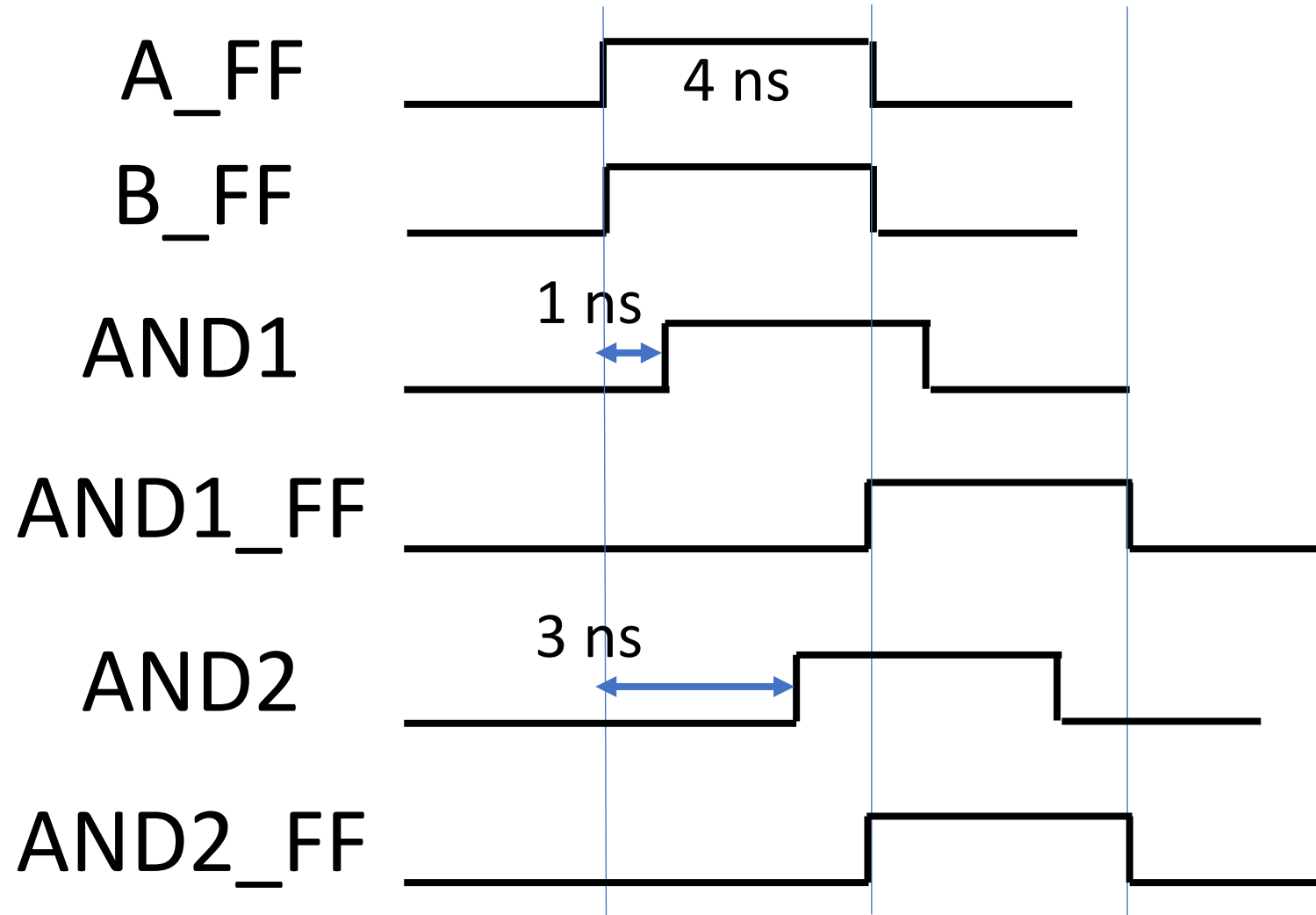

- AND with flipflops will output at same timing!

Implementing digital logic with FPGA

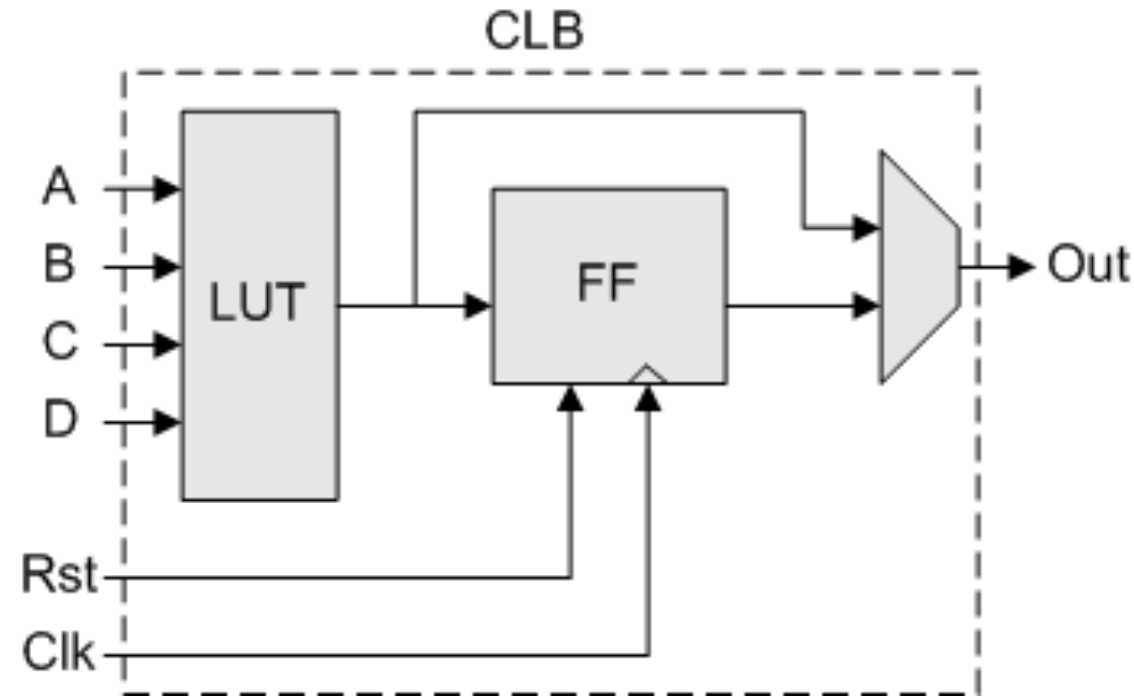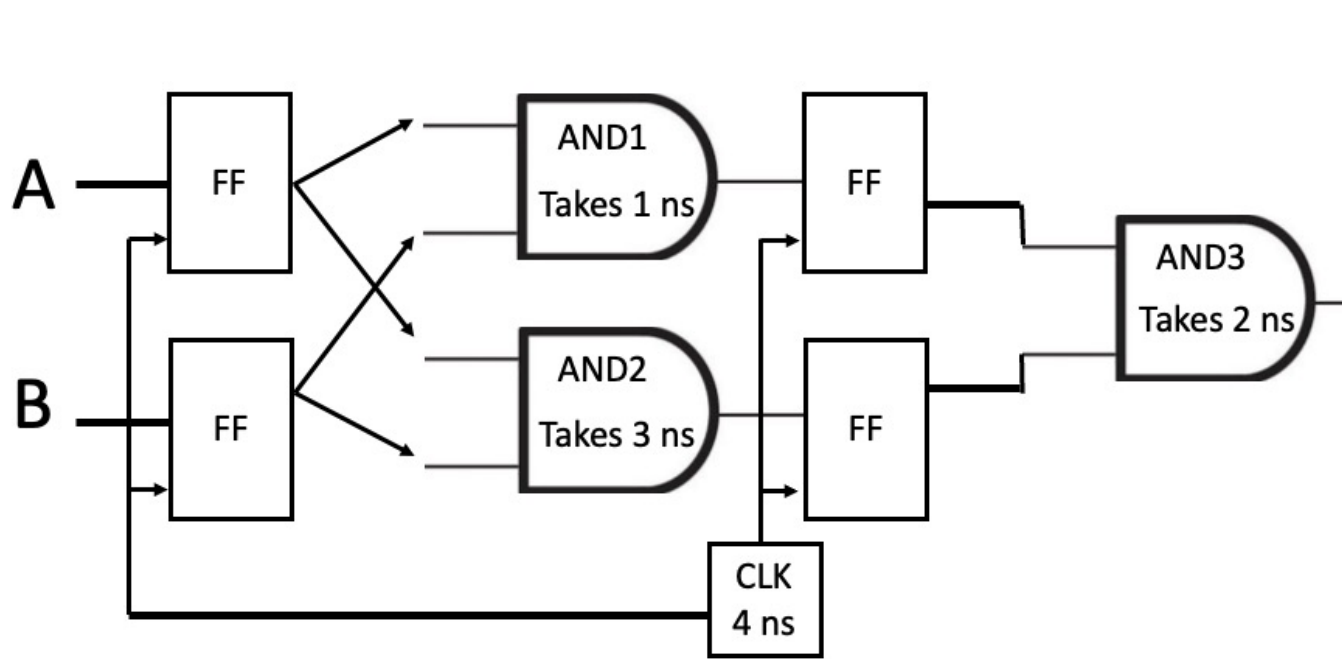


- Digital logic can be implemented with CLBs inside FPGA

➤ LUT become gates

➤ Flip-flops are inside CLBs


Flipflop timing requirements

 

su: Setup time
h: Hold time
cq: clock to q delay

- In reality, flop-flop also takes time to do things.
 - Input data needs to be stable during a clock edge.
 - Output also take time.

Flipflop timing requirements

 


su: Setup time
h: Hold time
cq: clock to q delay

- In reality, flop-flop also takes time to do things.
- So logic gates NEED to be quicker than one clock cycle.


What is firmware?

 - FPGA has many configurable components. (LUT, switch, ...)
 - Depending on configuration, functionality of FPGA changes.
- Configuration is set through “configuration memory”.





What is firmware?

 - Firmware has the data for the configuration memory.
- So firmware determines how the FPGA functions.



How can firmware be created?

  
- Need to create the data for the configuration memory.
- Need to know what the configurable components should be.



CLB-Configurable Logic Block
SM- Switch Matrix
IOB -Input and Output Block


How can firmware be created?

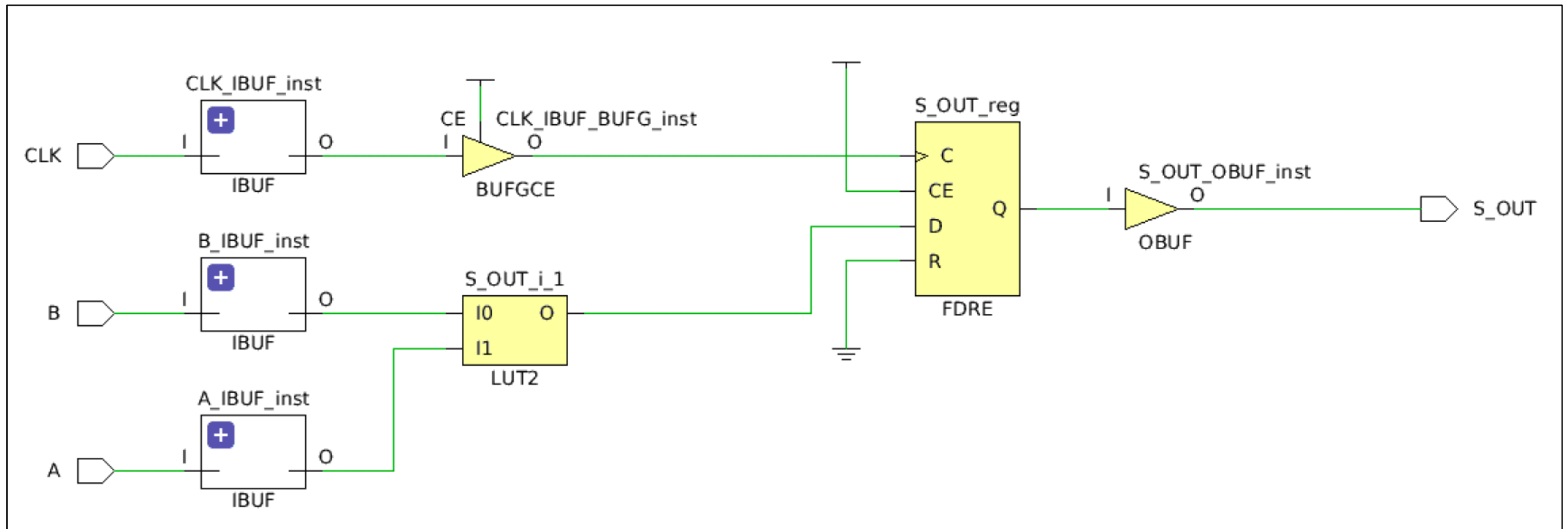- Need to know what resources should be used.
- Need to know connection between resources.
- Need convert logic into resources and connections.




How can firmware be created?

1. Design logic
2. Synthesis: Transforming logic into a netlist (gates and connections)
3. Implementation: Place and route the netlist onto device resources, within constraints.
4. Create bitstream (firmware file)

- ▼ SYNTHESIS
 - ▶ Run Synthesis
 - > Open Synthesized Design
- ▼ IMPLEMENTATION
 - ▶ Run Implementation
 - > Open Implemented Design
- ▼ PROGRAM AND DEBUG
 - ▶  Generate Bitstream
 - > Open Hardware Manager


Example of half adder

1. Design logic

 

Netlist


2. Synthesis

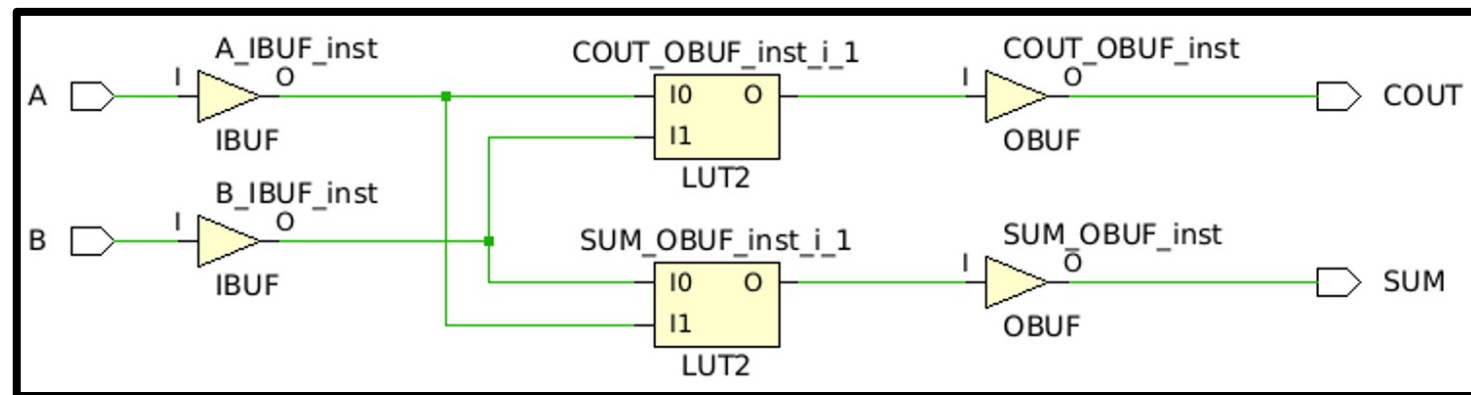

3. Implementation

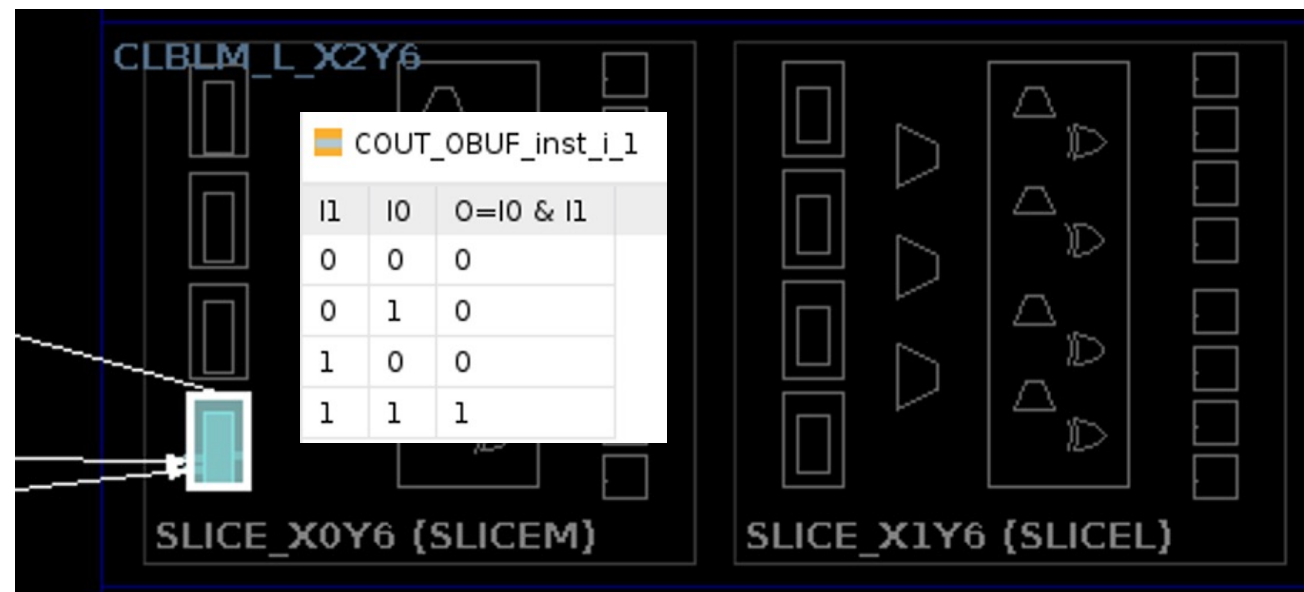4. Create bitstream

```
00000000: 0009 0ff0 0ff0 0ff0 0ff0 0000 0161 002c
00000010: 6861 6c66 5f61 6464 6572 3b55 7365 7249
00000020: 443d 3058 4646 4646 4646 4646 3b56 6572
00000030: 7369 6f6e 3d32 3032 342e 3100 6200 0c37
00000040: 7a30 3230 636c 6734 3030 0063 000b 3230
00000050: 3235 2f30 382f 3130 0064 0009 3139 3a30
00000060: 313a 3235 0065 003d bafc ffff ffff ffff
```



How much did you understand?

- www.kahoot.it